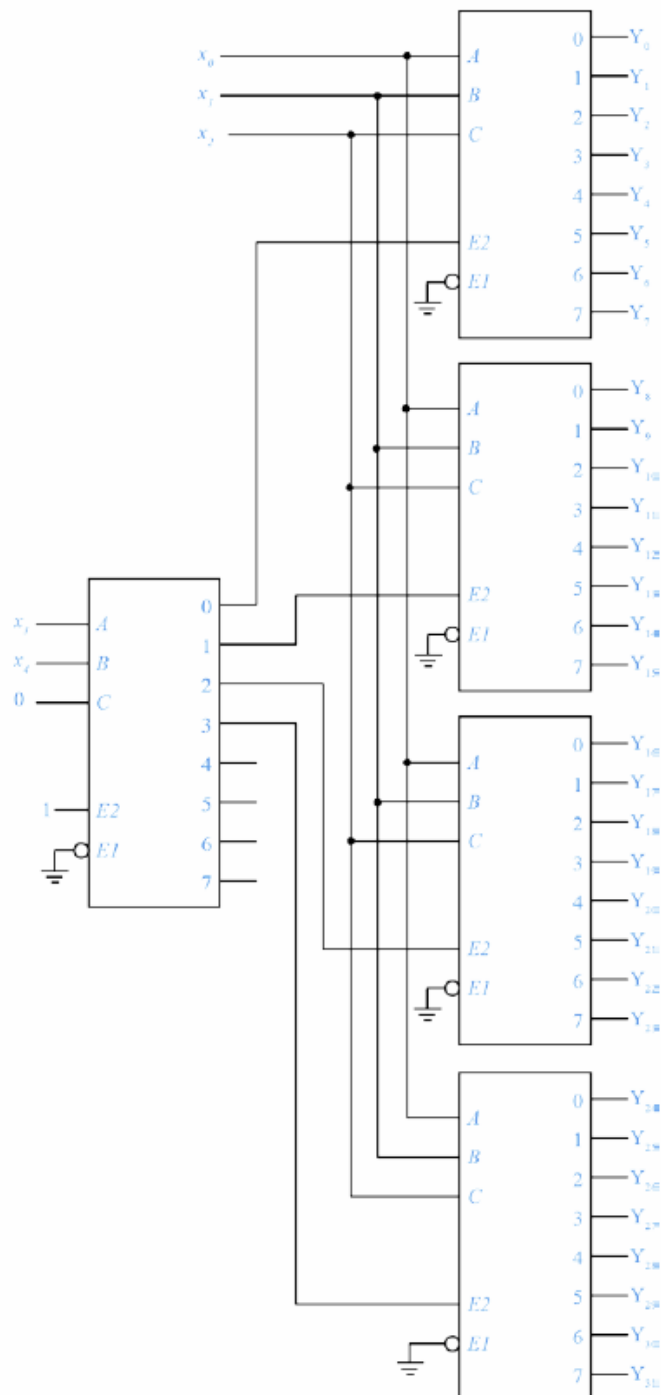


Homework Assignment 6 Solution

Prob 1:

Textbook 3.39 (inputs = $\{X_4 X_3 \dots X_1 X_0\}$; Decoder inputs $\{C B A\}$ C = msb)

3.39 Design a 5-to-32 decoder using 3-to-8 decoder modules as building blocks. Assume each 3-to-8 decoder has one active-low enable input, \overline{E}_1 , and one active-high enable input, E_2 .




Prob 2:


Textbook 3.40

3.40 Realize each of the following sets of functions using a 4-to-16 decoder module and output logic gates (choose NAND or AND gates to minimize the fan-in of the output gates).

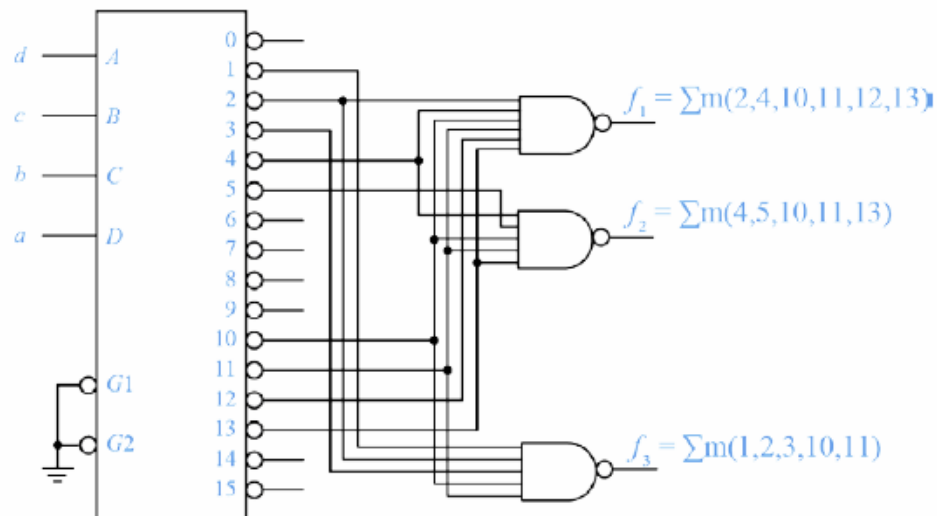
- (a) $f_1(a, b, c, d) = \sum m(2, 4, 10, 11, 12, 13)$
 $f_2(a, b, c, d) = \prod M(0, 3, 6, 9, 12, 14, 15) = \sum m(4, 5, 10, 11, 13)$
 $f_3(a, b, c, d) = \bar{b}c + \bar{a}\bar{b}d = \sum m(1, 2, 3, 10, 11)$



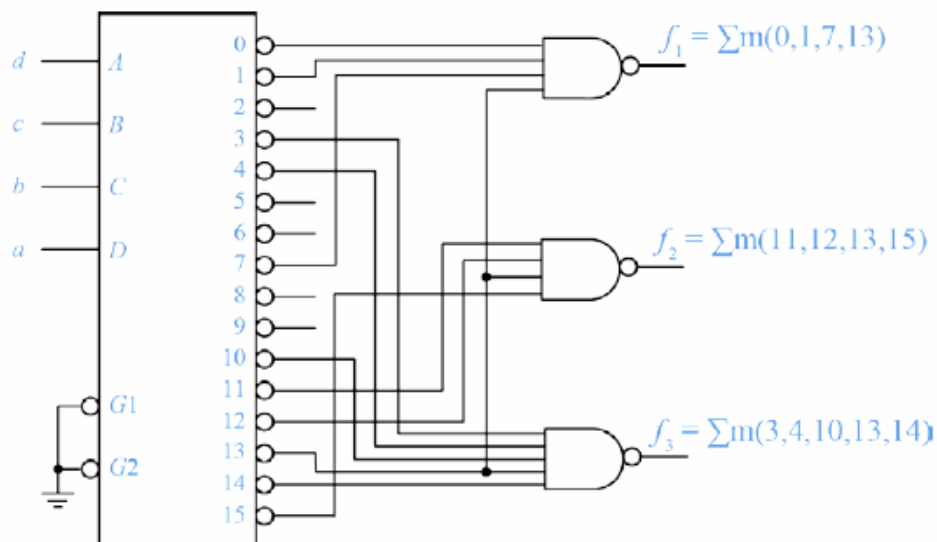
- (b) $f_1(a, b, c, d) = \sum m(0, 1, 7, 13)$
 $f_2(a, b, c, d) = ab\bar{c} + acd = \sum m(11, 12, 13, 15)$
 $f_3(a, b, c, d) = \prod M(0, 1, 2, 5, 6, 7, 8, 9, 11, 12, 15) = \sum m(3, 4, 10, 13, 14)$



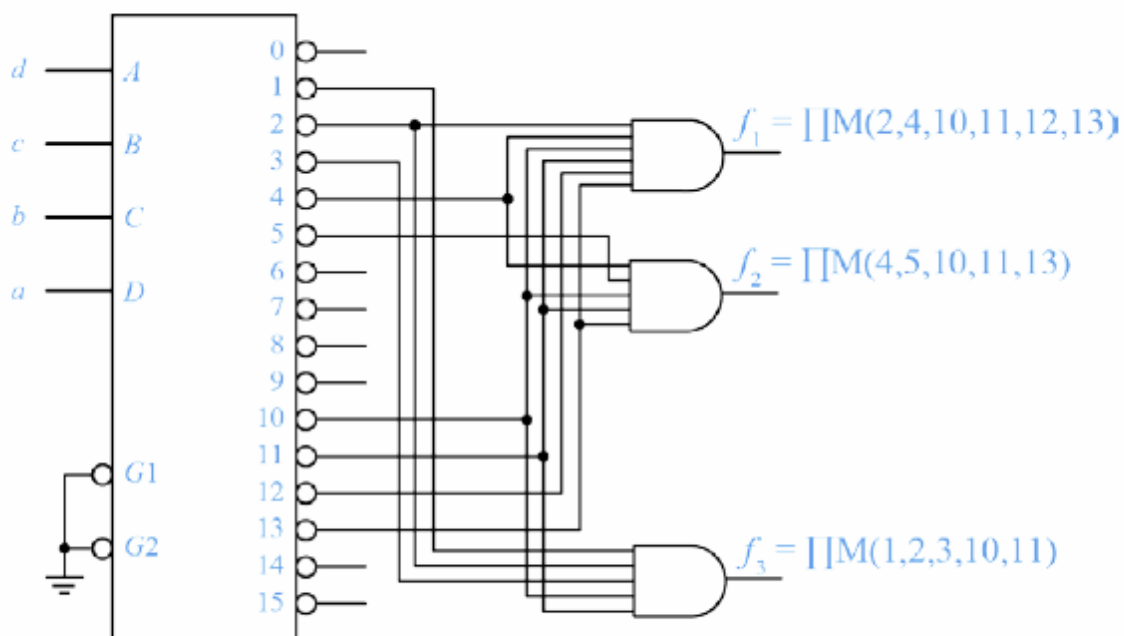(c) Repeat part (a) for the complements of the three functions.




(d) Repeat part (b) for the complements of the three functions.

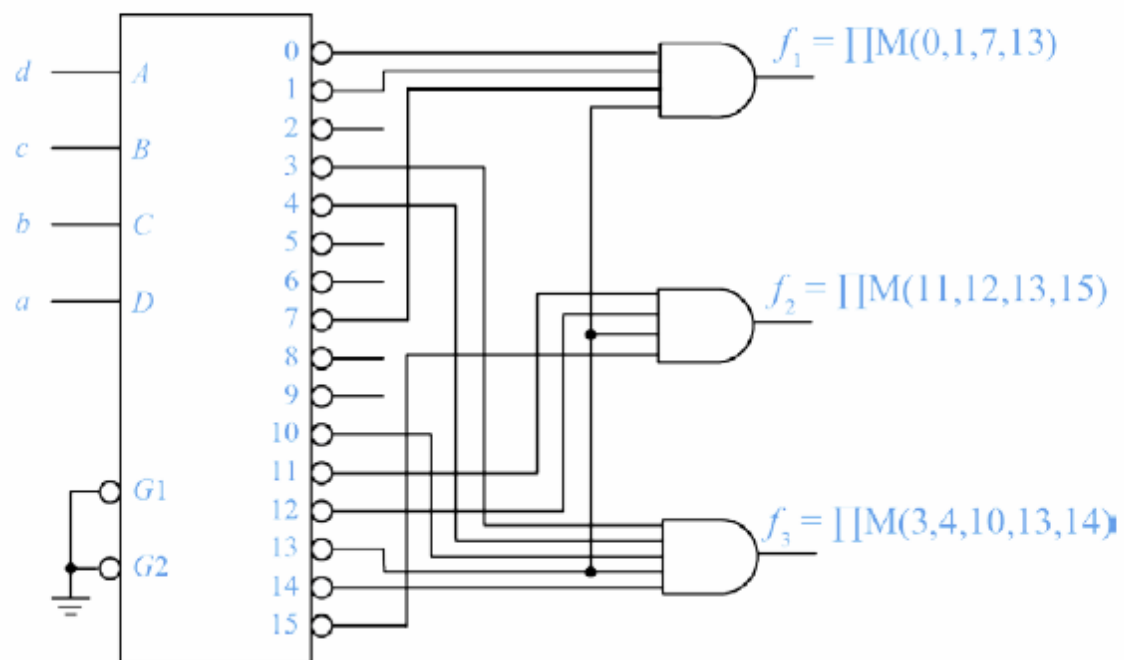


Prob 3: Textbook 3.61

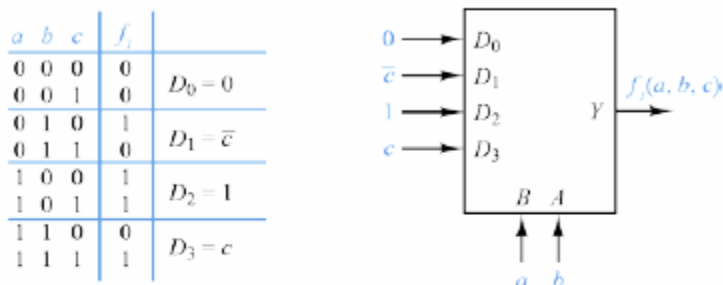3.61 Realize each of the following functions with a 4-to-1 multiplexer module.


$$\begin{aligned} \text{(a)} f_1(a, b, c) &= \sum m(2, 4, 5, 7) \\ &= \bar{a}b\bar{c} + a\bar{b}\bar{c} + a\bar{b}c + abc \\ &= (\bar{a}\bar{b}) \cdot 0 + (\bar{a}b)\bar{c} + (a\bar{b}) \cdot 1 + (ab)c \end{aligned}$$


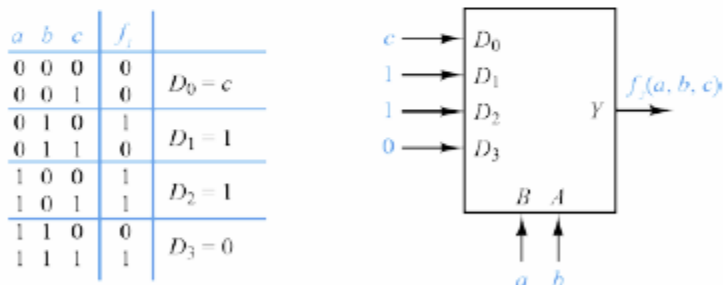
$$\begin{aligned} \text{(b)} f_2(a, b, c) &= \prod M(0, 6, 7) = \sum m(1, 2, 3, 4, 5) \\ &= \bar{a}\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + a\bar{b}\bar{c} + a\bar{b}c \\ &= (\bar{a}\bar{b})c + (\bar{a}b) \cdot 1 + (a\bar{b}) \cdot 1 + (ab) \cdot 0 \end{aligned}$$




$$\begin{aligned} \text{(c)} f_3(a, b, c) &= (a + \bar{b})(\bar{b} + c) \\ &= (a + \bar{b} + \bar{c})(a + \bar{b} + c)(\bar{a} + \bar{b} + c)(a + \bar{b} + c) \\ &= \prod M(2, 3, 6, 7) = \sum m(0, 1, 4, 5, 7) \\ &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + a\bar{b}c + abc \\ &= (\bar{a}\bar{b}) \cdot 1 + (\bar{a}b) \cdot 0 + (a\bar{b}) \cdot 1 + (ab)c \end{aligned}$$

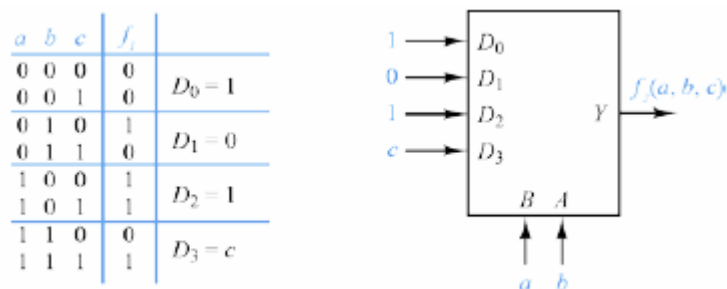


Prob 4: Textbook 3.62

3.62 Realize each of the following functions with an 8-to-1 multiplexer module.

(a) $f(b, c, d) = \sum m(0, 2, 3, 5, 7)$

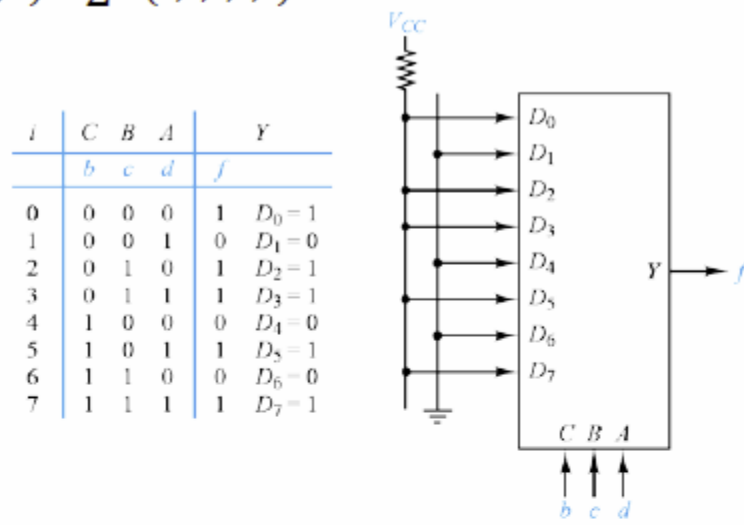


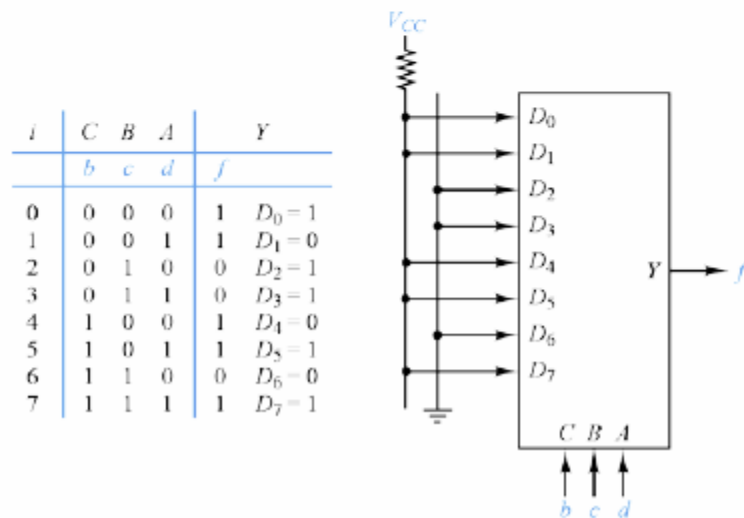(b) $f(b, c, d) = \bar{c} + b = (b + \bar{c} + \bar{d})(b + \bar{c} + d)$
 $= \prod M(2, 3) = \sum m(0, 1, 4, 5, 7)$



$$(c) f(a, b, c, d) = \prod M(0,1,2,3,6,7,8,9,12,14,15)$$

i	C	B	A	Y	
	a	b	c	d	f
0	0	0	0	0	0 $D_0=0$
1	0	0	0	1	0
2	0	0	1	0	0 $D_1=0$
3	0	0	1	1	0
4	0	1	0	0	1 $D_2=1$
5	0	1	0	1	1
6	0	1	1	0	0 $D_3=0$
7	0	1	1	1	0
8	1	0	0	0	0 $D_4=0$
9	1	0	0	1	0
10	1	0	1	0	1 $D_5=1$
11	1	0	1	1	1
12	1	1	0	0	0 $D_6=a$
13	1	1	0	1	1
14	1	1	1	0	0 $D_7=0$
15	1	1	1	1	0

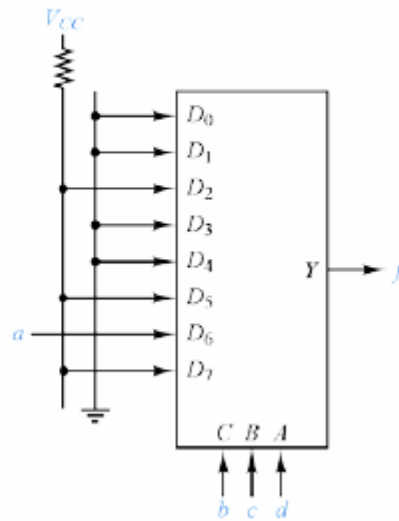

Prob 5: Textbook 3.68

3.68 Design a full adder module with data inputs A and B , carry input C_{in} , sum output S , and carry output C_{out} .

ABC_{in}	$C_{out}S$
000	0 0
001	0 1
010	0 1
011	1 0
100	0 1
101	1 0
110	1 0
111	1 1

(a) Use a 3-to-8 decoder and NAND gates (b) Use a four-input, 2-bit multiplexer

